


Chương 5

Thiết kế hệ vi xử lý

5.6 Giao tiếp bộ hiển thị (Display)

5.6.2 Giao tiếp với LCD

LCD controller

 

```

void WriteChar(char c){
    RS = 1;           /* indicate data being sent */
    DATA_BUS = c;   /* send data to LCD */
    EnableLCD(45);   /* toggle the LCD with appropriate delay */
}
    
```

CODES	
I/D = 1 cursor moves left	DL = 1 8-bit
I/D = 0 cursor moves right	DL = 0 4-bit
S = 1 with display shift	N = 1 2 rows
S/C = 1 display shift	N = 0 1 row
S/C = 0 cursor movement	F = 1 5x10 dots
R/L = 1 shift to right	F = 0 5x7 dots
R/L = 0 shift to left	

RS	R/W	DB ₇	DB ₆	DB ₅	DB ₄	DB ₃	DB ₂	DB ₁	DB ₀	Description
0	0	0	0	0	0	0	0	0	1	Clears all display, return cursor home
0	0	0	0	0	0	0	0	1	*	Returns cursor home
0	0	0	0	0	0	0	1	I/D	S	Sets cursor move direction and/or specifies not to shift display
0	0	0	0	0	0	1	D	C	B	ON/OFF of all display(D), cursor ON/OFF (C), and blink position (B)
0	0	0	0	0	1	S/C	R/L	*	*	Move cursor and shifts display
0	0	0	0	1	DL	N	F	*	*	Sets interface data length, number of display lines, and character font
1	0	WRITE DATA								Writes Data

LCD Operation

LCD is gaining popular and replacing LEDs (7-segment ...), due to

1. declining price
2. the ability to display numbers, characters, and graphics
3. relieving the CPU task by incorporating a refreshing controller
4. ease of programming for characters and graphics (OLED is the coming display)

LCD Pin Descriptions

- 14-pin LCD module is discussed here, table 12-1 lists pin's function, Fig 12-1 shows the pin positions for various LCDs
- Vcc, Vss provide +5V and ground
 - Vee is used for contrast controlling
 - RS (register select) is used to select the instruction command code register (RS = 0) or data register (RS = 1)
 - LCD command codes is listed at table 12-2
 - R/W (read/write) allows user to write to (R/W = 0) or read from (R/W = 1) information
 - E (enable) latch information at data pins; when data is supplied to data pins, a high-to-low pulse must be applied to this pin
 - D0-D7 are the 8-bit data pins; send information to LCD (R/W = 0) and read contents of LCD internal registers (R/W = 1)
 - to display letters and numbers, ASCII codes are sent while RS = 1

Table 12-1. Pin Descriptions for LCD


Pin	Symbol	I/O	Description
1	V_{SS}	--	Ground
2	V_{CC}	--	+5V power supply
3	V_{EE}	--	Power supply to control contrast
4	RS	I	RS=0 to select command register, RS=1 to select data register
5	R/W	I	R/W=0 for write, R/W=1 for read
6	E	I/O	Enable
7	DB0	I/O	The 8-bit data bus
8	DB1	I/O	The 8-bit data bus
9	DB2	I/O	The 8-bit data bus
10	DB3	I/O	The 8-bit data bus
11	DB4	I/O	The 8-bit data bus
12	DB5	I/O	The 8-bit data bus
13	DB6	I/O	The 8-bit data bus
14	DB7	I/O	The 8-bit data bus

Table 12-2: LCD Command Codes


Code	Command to LCD Instruction
(Hex)	Register
1	Clear display screen
2	Return home
4	Decrement cursor (shift cursor to left)
6	Increment cursor (shift cursor to right)
5	Shift display right
7	Shift display left
8	Display off, cursor off
A	Display off, cursor on
C	Display on, cursor off
E	Display on, cursor blinking
F	Display on, cursor blinking
10	Shift cursor position to left
14	Shift cursor position to right
18	Shift the entire display to the left
1C	Shift the entire display to the right
80	Force cursor to beginning of 1st line
C0	Force cursor to beginning of 2nd line
38	2 lines and 5x7 matrix

Note: This table is extracted from Table 12-4.


Pin diagrams

 

DMC1610A
DMC1606C
DMC16117
DMC16128
DMC16129
DMC1616433
DMC20434

 

DMC16106B
DMC16207
DMC16230
DMC20215
DMC32216

 

DMC20261
DMC24227
DMC24138
DMC32132
DMC32239
DMC40131
DMC40218

- RS = 0, the command code register is selected, we can send instruction to LCD to perform clear, shift, blink ...
- when RS = 0, and R/W = 1, D7 is busy flag, when D7 = 0, LCD is ready to receive new information; it is recommended to check the busy flag before writing any data to the LCD

LCD Interfacing

- Liquid Crystal Displays (LCDs) have become a cheap and easy way to display text for an embedded system
 - Various configurations (1 line by 20 characters upto 8 lines by 80 characters).
- LCD needs a driving circuit to work.
- Driving circuit and LCD are often integrated into a single chip Hitachi LM015 can display one line of 16 characters
- The display has one register into which commands are sent and one register into which data to be displayed are sent
- Two registers are differentiated by the RS input
- Data lines (DB7-DB0) are used to transfer both commands (clearing, cursor positioning, etc) and data (character to be displayed)

Alphanumeric LCD Interfacing

Microcontroller

- **Pinout**

- 8 data pins D7:D0
- RS: Data or Command Register Select
- R/W: Read or Write
- E: Enable (Latch data)

- **RS** – Register Select

- RS = 0 → Command Register
- RS = 1 → Data Register


- **R/W** = 0 → Write, R/W = 1 → Read

- **E** – Enable

- Used to latch the data present on the data pins.

- **D0 – D7**

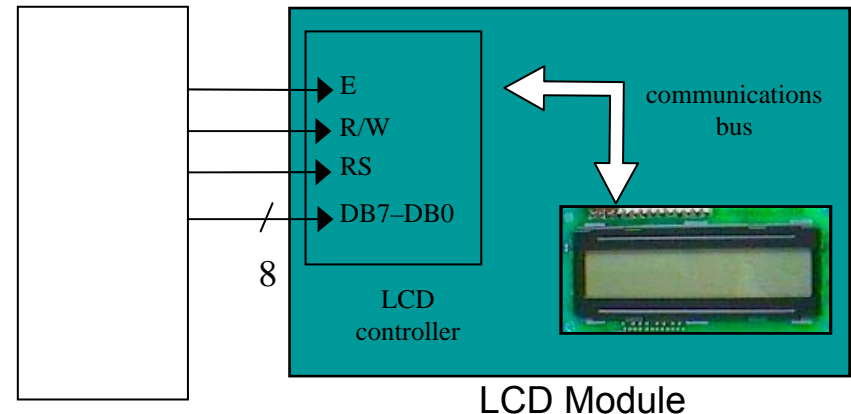
- Bi-directional data/command pins.
- Alphanumeric characters are sent in ASCII format.



LCD Commands

- The LCD's internal controller can accept several commands and modify the display accordingly. These commands would be things like:
 - Clear screen
 - Return home
 - Decrement/Increment cursor
- After writing to the LCD, it takes some time for it to complete its internal operations. During this time, it will not accept any new commands or data.
 - We need to insert time delay between any two commands or data sent to LCD

Interfacing LCD with 8051

 

Interfacing LCD with 8051

In main program:

```
...  
MOV  A, COMMAND  
CALL  CMD  
CALL DELAY  
MOV  A, ANOTHER_CMD  
CALL  CMD  
CALL DELAY  
MOV  A, #'A'  
CALL  DATA  
CALL DELAY  
MOV  A, #'B'  
CALL  DATA  
CALL DELAY .....
```

Command and Data Write Routines

```
DATA: MOV  P1, A ; A is ascii data  
      SETB P3.3 ; RS=1 data  
      CLR  P3.4 ; RW=0 for write  
      SETB P3.5 ; H->L pulse on E  
      CLR  P3.5  
      RET
```

```
CMD:  MOV  P1, A ; A has the cmd word  
      CLR  P3.3 ; RS=0 for cmd  
      CLR  P3.4 ; RW=0 for write  
      SETB P3.5 ; H->L pulse on E  
      CLR  P3.5  
      RET
```

Sending code or data to the LCD with checking busy flag

The above code showed how to send commands to the LCD without checking the busy flag. Notice that we must put a long delay in between issuing data or commands to the LCD. However, a much better way is to monitor the busy flag before issuing a command or data to the LCD. This is shown below.

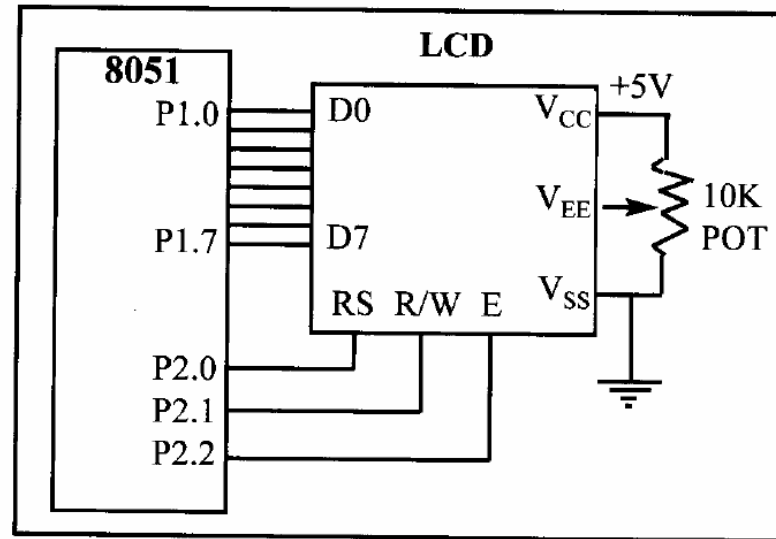


Figure 12-2. LCD Connection

```
;Check busy flag before sending data, command to LCD
;P1=data pin
;P2.0 connected to RS pin
;P2.1 connected to R/W pin
;P2.2 connected to E pin
      ORG
      MOV     A,#38H ;init. LCD 2 lines,5x7 matrix
      ACALL  COMMAND ;issue command
      MOV     A,#0EH ;LCD on, cursor on
      ACALL  COMMAND ;issue command
      MOV     A,#01H ;clear LCD command
      ACALL  COMMAND ;issue command
      MOV     A,#06H ;shift cursor right
      ACALL  COMMAND ;issue command
      MOV     A,#86H ;cursor: line 1, pos. 6
      ACALL  COMMAND ;command subroutine
```

```

        MOV     A, #'N'           ;display letter N
        ACALL  DATA_DISPLAY
        MOV     A, #'0'           ;display letter 0
        ACALL  DATA_DISPLAY
HERE:    SJMP   HERE             ;STAY HERE
COMMAND: ACALL  READY            ;is LCD ready?
        MOV     P1,A             ;issue command code
        CLR     P2.0             ;RS=0 for command
        CLR     P2.1             ;R/W=0 to write to LCD
        SETB    P2.2             ;E=1 for H-to-L pulse
        CLR     P2.2             ;E=0 ,latch in
        RET
DATA_DISPLAY:
        ACALL  READY            ;is LCD ready?
        MOV     P1,A             ;issue data
        SETB    P2.0             ;RS=1 for data
        CLR     P2.1             ;R/W=0 to write to LCD
        SETB    P2.2             ;E=1 for H-to-L pulse
        CLR     P2.2             ;E=0, latch in
        RET

```

READY:

```
    SETB    P1.7          ;make P1.7 input port
    CLR     P2.0          ;RS=0 access command reg
    SETB    P2.1          ;R/W=1 read command reg
;read command reg and check busy flag
BACK:CLR    P2.2          ;E=1 for H-to-L pulse
    SETB    P2.2          ;E=0 H-to-L pulse
    JB     P1.7, BACK     ;stay until busy flag=0
    RET
    END
```

Notice in the above program that the busy flag is D7 of the command register. To read the command register we make $R/W = 1$, $RS = 0$, and a H-to-L pulse for the E pin will provide us the command register. After reading the command register, if bit D7 (the busy flag) is high, the LCD is busy and no information (command or data) should be issued to it. Only when $D7 = 0$ can we send data or commands to the LCD. Notice in this method that there are no time delays used since we are checking the busy flag before issuing commands or data to the LCD.

LCD data sheet

In the LCD, one can put data at any location. The following shows address locations and how they are accessed.

RS	R/W	DB7	DB6	DB5	DB4	DB3	DB2	DB1	DB0
0	0	1	A	A	A	A	A	A	A

where AAAAAAAAA = 0000000 to 0100111 for line 1 and AAAAAAAAA = 1000000 to 1100111 for line 2. See Table 12-3.

Table 12-3: LCD Addressing

	DB7	DB6	DB5	DB4	DB3	DB2	DB1	DB0
Line 1 (min)	1	0	0	0	0	0	0	0
Line 1 (max)	1	0	1	0	0	1	1	1
Line 2 (min)	1	1	0	0	0	0	0	0
Line 2 (max)	1	1	1	0	0	1	1	1

The upper address range can go as high as 0100111 for the 40-character-wide LCD while for the 20-character-wide LCD it goes up to 010011 (19 decimal = 10011 binary). Notice that the upper range 0100111 (binary) = 39 decimal which corresponds to locations 0 to 39 for the LCDs of 40x2 size.


From the above discussion we can get the addresses of cursor positions for various sizes of LCDs. See Figure 12-3. Note that all the addresses are in hex. Figure 12-4 gives a diagram of LCD timing. Table 12-4 provides a detailed list of LCD commands and instructions. Table 12-2 is extracted from this table.

LCD

16 x 2 LCD	80	81	82	83	84	85	86 through 8F
	C0	C1	C2	C3	C4	C5	C6 through CF
20 x 1 LCD	80	81	82	83	through 93		
20 x 2 LCD	80	81	82	83	through 93		
	C0	C1	C2	C3	through D3		
20 x 4 LCD	80	81	82	83	through 93		
	C0	C1	C2	C3	through D3		
	94	95	96	97	through A7		
	D4	D5	D6	D7	through E7		
40 x 2 LCD	80	81	82	83	through A7		
	C0	C1	C2	C3	through E7		
<i>Note: All data is in hex.</i>							

Figure 12-3 Cursor Addresses for Some LCDs

LCD Timing

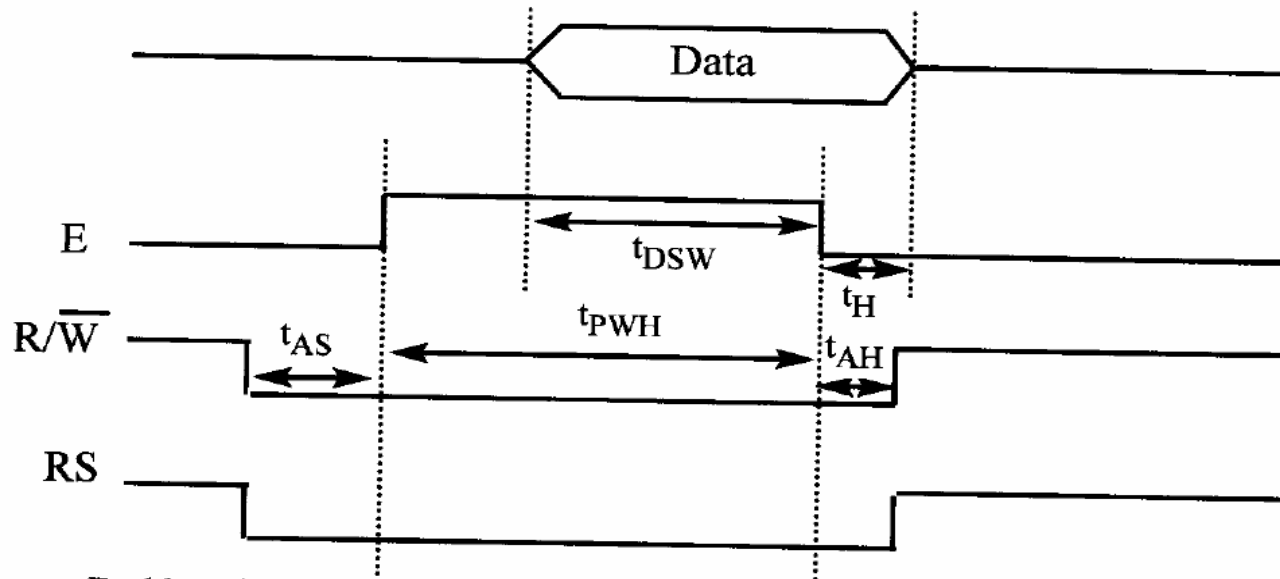

t_{PWH} = Enable pulse width = 450 ns (minimum)

t_{DSW} = Data set up time = 195 ns (minimum)

t_H = Data hold time = 10 ns (minimum)

t_{AS} = Set up time prior to E (going high) for both RS and R/W = 140 ns (minimum)

t_{AH} = Hold time after E has come down for both RS and R/W = 10 ns (minimum)

Figure 12-4: LCD Timing

Table 12-4: List of LCD Instructions

Instruction	RS	R/W	DB7	DB6	DB5	DB4	DB3	DB2	DB1	DB0	Description	Execution Time (Max)
Clear Display	0	0	0	0	0	0	0	0	0	1	Clears entire display and sets DD RAM address 0 in address counter	1.64 ms
Return Home	0	0	0	0	0	0	0	0	1	-	Sets DD RAM address 0 as address counter. Also returns display being shifted to original position. DD RAM contents remain unchanged.	1.64 ms
Entry Mode Set	0	0	0	0	0	0	0	1	1/D	S	Sets cursor move direction and specifies shift of display. These operations are performed during data write and read.	40 μ s
Display On/Off Control	0	0	0	0	0	0	0	1	D	C B	Sets On/Off of entire display (D), cursor On/Off (C), and blink of cursor position character (B).	40 μ s
Cursor or Display Shift	0	0	0	0	0	0	1	S/C	R/L	- -	Moves cursor and shifts display without changing DD RAM contents.	40 μ s
Function Set	0	0	0	0	1	DL	N	F	-	-	Sets interface data length (DL), number of display lines (L) and character font (F).	40 μ s

Set CG RAM Address	0 0 0 1	AGC	Sets CG RAM address. CG RAM data is sent and received after this setting.	40 μ s
Set DD RAM Address	0 0 1	ADD	Sets DD RAM address. DD RAM data is sent and received after this setting.	40 μ s
Read Busy Flag & Address	0 1 BF	AC	Reads Busy flag (BF) indicating internal operation is being performed and reads address counter contents.	40 μ s
Write Data CG or DD RAM	1 0	Write Data	Writes data into DD or CG RAM.	40 μ s
Read Data CG or DD RAM	1 1	Read Data	Reads data from DD or CG RAM.	40 μ s

Notes:

1. Execution times are maximum times when fcp or fosc is 250 kHz.
2. Execution time changes when frequency changes. Ex: When fcp or fosc is 270 kHz: $40 \mu\text{s} \times 250 / 270 = 37 \mu\text{s}$.
3. Abbreviations:

DD RAM	Display data RAM	
CG RAM	Character generator RAM	
ACC	CG RAM address	
ADD	DD RAM address, corresponds to cursor address	
AC	Address counter used for both DD and CG RAM addresses.	
I/D = 1	Increment	I/D = 0 Decrement
S=1	Accompanies display shift	
S/C = 1	Display shift;	S/C = 0 Cursor move
R/L = 1	Shift to the right;	R/L = 0 Shift to the left
DL = 1	8 bits, DL = 0: 4 bits	
N = 1	1 line, N = 0 : 1 line	
F = 1	5 x 10 dots, F = 0 : 5 x 7 dots	
BF = 1	Internal operation;	BF = 0 Can accept instruction

Stepper Motors

- more accurately controlled than a normal motor allowing fractional turns or n revolutions to be easily done
- low speed, and lower torque than a comparable D.C. motor
- useful for precise positioning for robotics
- Servomotors require a position feedback signal for control

Stepper Motor Diagram

 


Figure 4-38. Rotor Alignment
(Courtesy of Superior Electric Company)

Stepper Motor Step Angles

**Table 4-12:
Stepper Motor
Step Angles**

Step Angle	Steps Per Revolution
0.72	500
1.8	200
2	180
2.5	144
5	72
7.5	48
15	24



Terminology

- Steps per second, RPM
 - $SPS = (RPM * SPR) / 60$
- Number of teeth
- 4-step, wave drive 4-step, 8-step
- Motor speed (SPS)
- Holding torque

Stepper Motor Types

- Variable Reluctance
- Permanent Magnet



Variable Reluctance Motors

  

Variable Reluctance Motors

- This is usually a four wire motor – the common wire goes to the +ve supply and the windings are stepped through
- Our example is a 30° motor
- The rotor has 4 poles and the stator has 6 poles





- **Example**

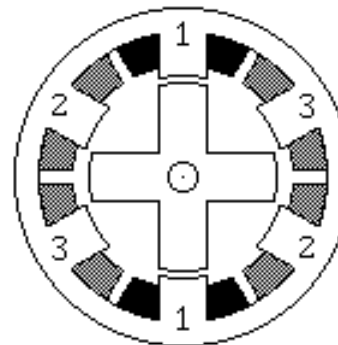 

Variable Reluctance Motors

- To rotate we excite the 3 windings in sequence
 - W1 - 1001001001001001001001001001
 - W2 - 0100100100100100100100100100
 - W3 - 0010010010010010010010010010
- This gives two full revolutions

Unipolar Motors

  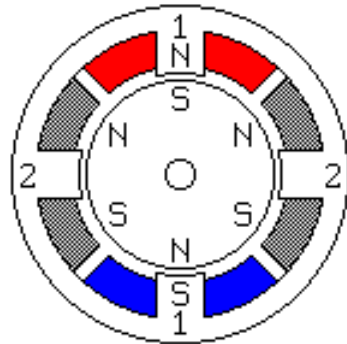 

Unipolar Motors

- To rotate we excite the 2 windings in sequence
 - W1a - 1000100010001000100010001
 - W1b - 00100010001000100010001000100
 - W2a - 01000100010001000100010001000
 - W2b - 00010001000100010001000100010
- This gives two full revolutions

Basic Actuation Wave Forms

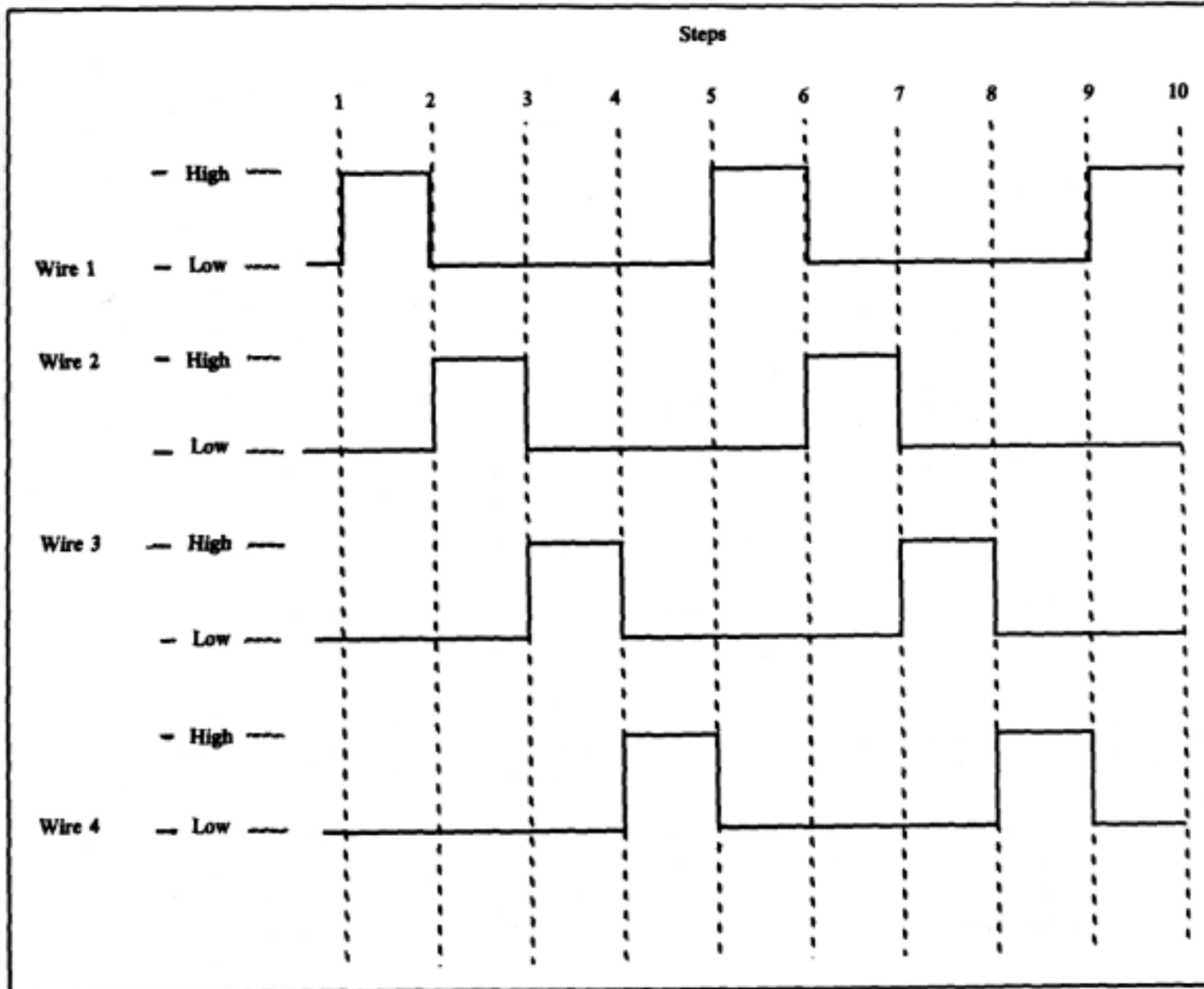


Fig. 14-4. The basic wave-step actuation sequence of a four-phase stepper motor.

Unipolar Motors

- To rotate we excite the 2 windings in sequence
 - W1a - 1100110011001100110011001
 - W1b - 0011001100110011001100110
 - W2a - 0110011001100110011001100
 - W2b - 1001100110011001100110011
- This gives two full revolutions at 1.4 times greater torque but twice the power

Enhanced Waveforms

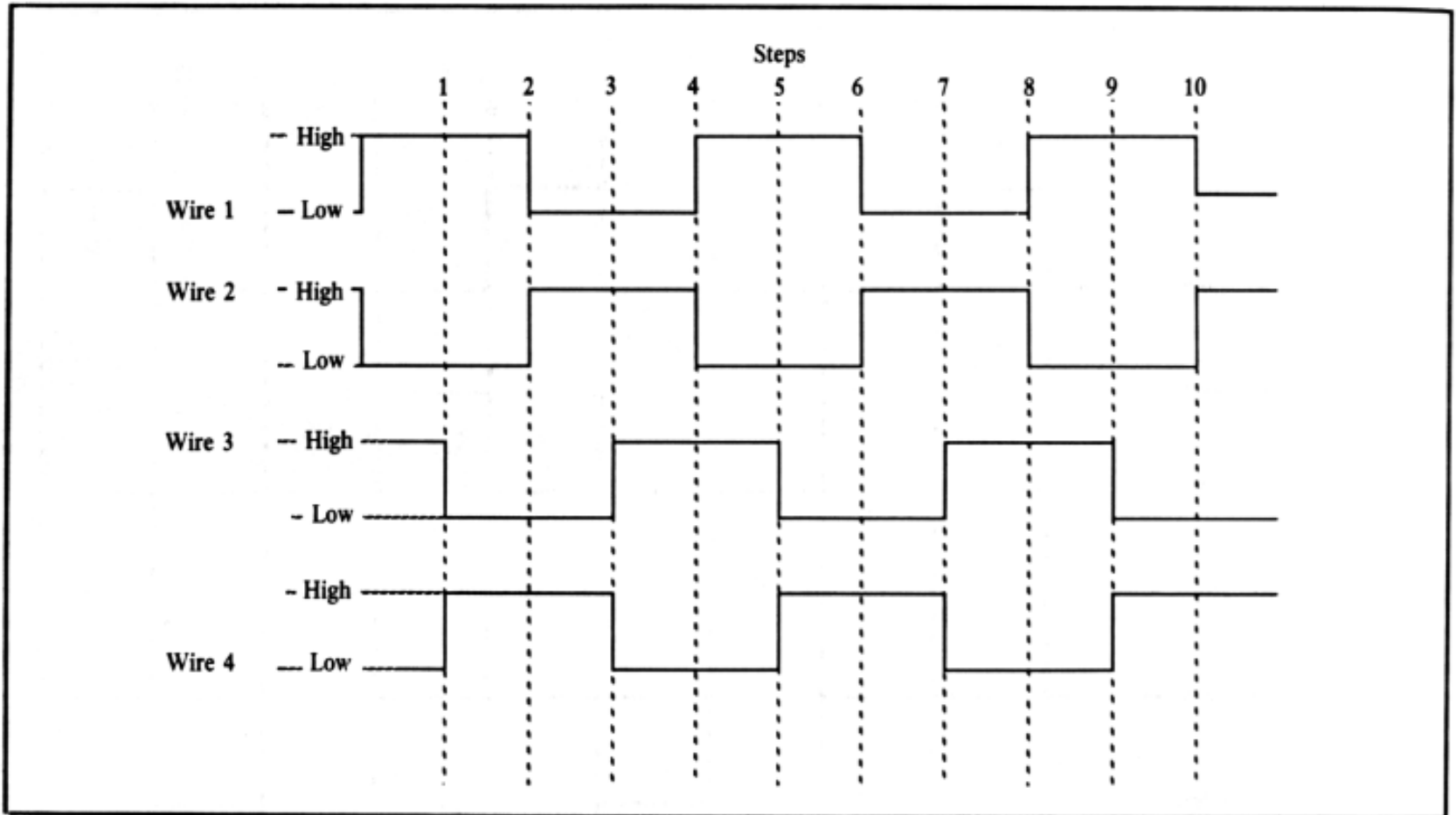


Fig. 14-5. The enhanced on-on/off-off actuation sequence of a four-phase stepper motor.


- better torque
- more precise control

Unipolar Motors

- The two sequences are not the same, so by combining the two you can produce half stepping
 - W1a - 11000001110000011100000111
 - W1b - 00011100000111000001110000
 - W2a - 01110000011100000111000001
 - W2b - 00000111000001110000011100

Motor Control Circuits

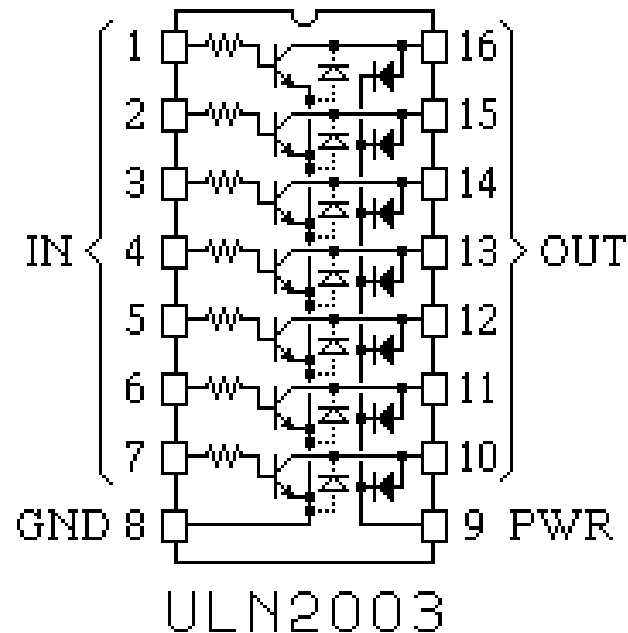- For low current options the ULN200x family of Darlington Arrays will drive the windings direct.



Interfacing to Stepper Motors

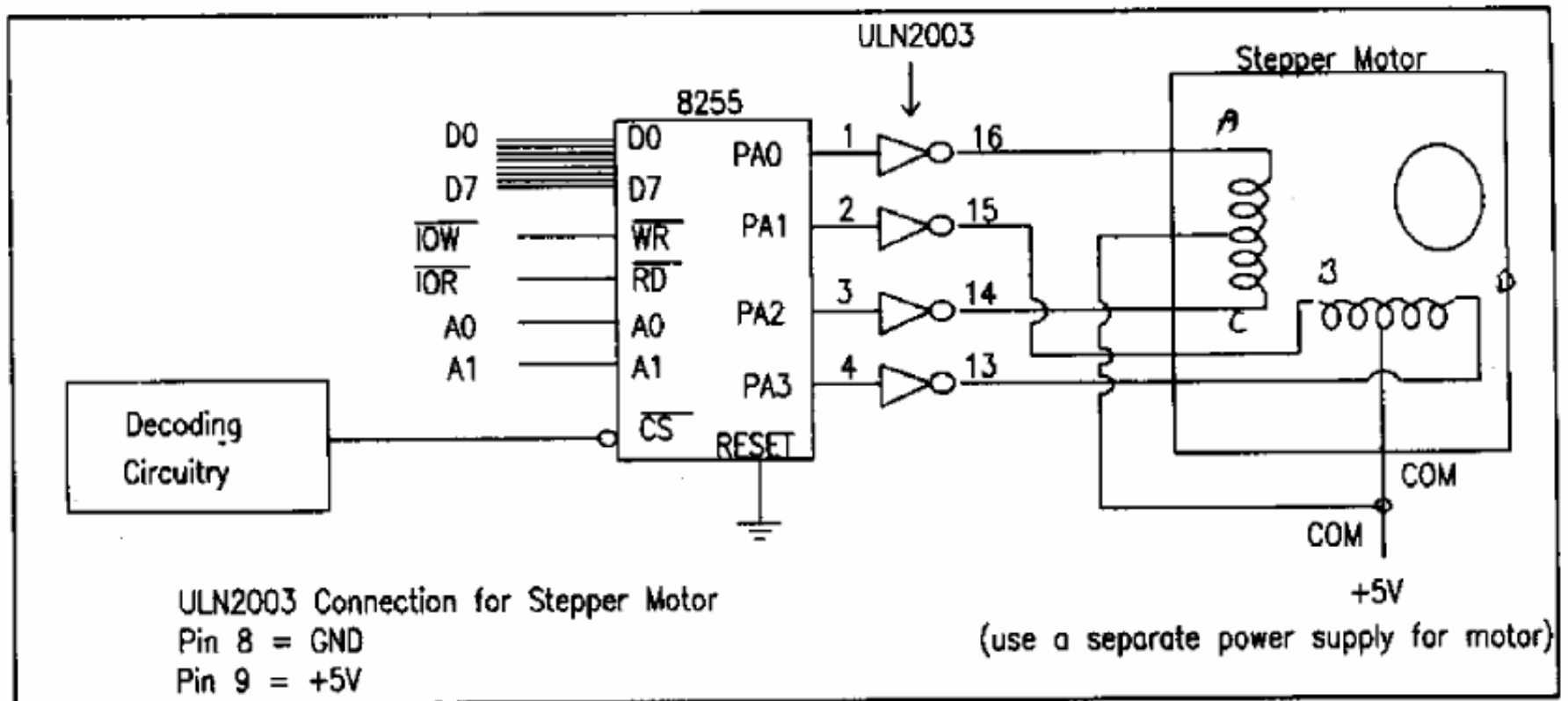


Figure 4-40. 8255 Connection to Stepper Motor

Example (với 80x86)

```
MOV    AL,80H           ;control word for all 8255 ports as out
MOV    DX,303H         ;control reg address of 8255 on PC Trainer
OUT    DX,AL           ;to control reg
MOV    BL,66H          ;or BL=33H, BL=99H or BL=0CCH
AGAIN: MOV    AH,01     ;check the key press
INT    16H             ;using INT 16
JNZ    EXIT            ;stop if any key pressed
MOV    AL,BL           ;otherwise send pulse to stepper motor
MOV    DX,300H         ;port A address of 8255 on PC Trainer
OUT    DX,AL
MOV    CX,0FFFFH       ;(change this value to see rotation speed)
HERE:  LOOP   HERE     ;wait for delay
ROR    BL,1            ;rotate for next step
JMP    AGAIN           ;and continue until a key is pressed
EXIT:
```

Giao tiếp với DAC

Digital-to-analog converters

- A digital-to-analogue converter (DAC) translates a digital value to analogue signals.
- The analogue output of an DAC is proportional to its digital input.
- The analogue signals could be voltage or current.
- Digital input can be entered via either a parallel or serial interface.

- Examples of DAC ICs
 - DAC0800: current mode, 8-bit, parallel interface.
 - MAX5521: voltage mode, 10-bit, serial interface.

DAC conversion equation


- Let's consider a n-bit **voltage-mode** DAC.
- Let $d = D_{n-1}D_{n-2} \dots D_0$ be the digital input to the DAC.
- Let V_{ref} be the input reference voltage.
- The output voltage produced by the DAC is

$$V_{out} = V_{ref} \left(\frac{D_{n-1}}{2} + \frac{D_{n-2}}{2^2} + \dots + \frac{D_2}{2^{n-2}} + \frac{D_1}{2^{n-1}} + \frac{D_0}{2^n} \right)$$

- In other words,

$$V_{out} = d \times \frac{V_{ref}}{2^n}$$


DAC example

 

Input-output plot of a 3-bit DAC

DAC designs


Weighted resistor design

 

$$-\frac{V_{ref} D_{n-1}}{2R} - \frac{V_{ref} D_{n-2}}{2^2 R} + \dots - \frac{V_{ref} D_0}{2^n R} + \frac{V_{out}}{R} = 0$$

- The weighted resistor design requires precise resistors over a wide range: very difficult to achieve.

R/2R ladder design

 

$$V_{out} = V_{ref} \left(\frac{D_{n-1}}{2} + \frac{D_{n-2}}{2^2} + \dots + \frac{D_0}{2^n} \right)$$

- The R-2R ladder design requires only two resistor values.

Parameters of a DAC

- **Number of bits:** $n = 8, 10, 12, 13, 14$, etc.

A larger n means smoother output.

- **Full scale value:** maximum output (i.e. when $d = 2^n - 1$)

$$V_{FS} = V_{ref} \times \frac{2^n - 1}{2^n}$$

- **Step size (resolution):** the smallest change that can be produced

$$step\ size = \frac{V_{ref}}{2^n}$$

- **Quantization error** is half of the step size.

- **Percentage resolution:**


$$percentage\ resolution = \frac{step\ size}{V_{FS}} = \frac{100\%}{2^n - 1}$$

Parameters of a DAC


- **Settling time**: time between the application of input and the output settling to within a specified band of the final value.
- **Offset error**: the nonzero DAC output when a 0 output is requested (by putting $d = 0$).
- **Full scale error**: the maximum deviation of the actual FS output from the expected FS output.
- **Linearity**: maximum deviation from the best-bit line for of input-output plot.
- **Monotonic**: increasing or decreasing input-output function.

Parameters of a DAC

3-bit voltage-mode DAC

 

DAC board

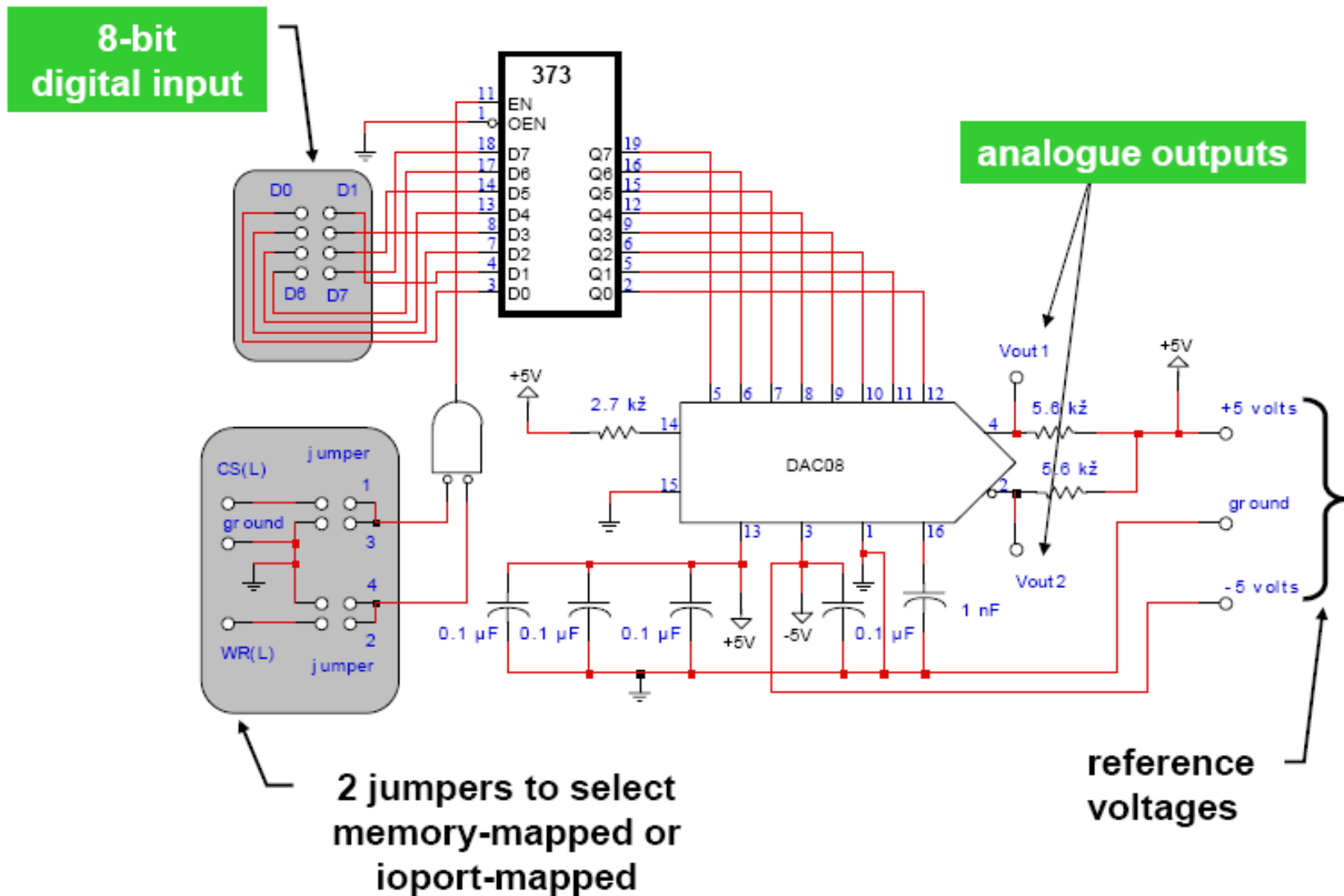

Digital to Analog Converter

 


Figure 4-42. DAC Connection to 8255

Resolution: 8 bit

Example – Step Ramp

Example 4-18

In order to generate a stair-step ramp, set up the circuit in Figure 4-42 and connect the output to an oscilloscope. Then write a program to send data to the DAC to generate a stair-step ramp.

Solution:

```
      MOV  AL,80H      ;all ports as output
      MOV  DX,303H    ;control reg address of PC Trainer
      OUT  DX,AL
A1:   MOV  AH,01      ;check for key press
      INT  16H       ;using PC BIOS INT 16
      JNZ  STOP      ;stop if any key is pressed
      SUB  AL,AL     ;other wise generate a stair-step ramp
      MOV  DX,300H
A2:   OUT  DX,AL
      INC  AL        ;next step
      CMP  AL,0      ;
      JZ   A1        ;if zero check for the key press
      MOV  CX,02FFH ;delay (for fast CPUs increase value in CX)
WT:   LOOP WT        ;let DAC recover
      JMP  A2        ;create next step
STOP: MOV  AH,4CH    ;go to DOS
      INT  21H
```

Giao tiếp với ADC

Analogue to digital converter

- An ADC samples an analogue signal at discrete times and converts the sampled signal to digital form.

- Used with transducers, ADCs allow us to monitor real-world inputs and perform control based on the inputs.

- Examples of ADC ICs
 - ADC0804: 8-bit, successive approximation
 - Maxim104: 8-bit, flash type

ADC applications

■ Local positioning sensor for object tracking

- ❑ The Receiver Signal Strength Indicator (RSSI) output of an FM receiver is measured.
- ❑ The RSSI output voltage is inversely proportional to the distance.

■ Temperature sensor for controlling shower water

- ❑ We can measure the output voltage of a thermistor.
- ❑ The thermistor's resistance depends on its temperature.

■ Electric fence monitoring

- ❑ Measure the voltage level of an electric fence.
- ❑ Determine if the fence is being tampered.

ADC conversion equation

- Let's consider an n-bit ADC.
- Let V_{ref} be the reference voltage.
- Let V_{in} be the analogue input voltage.


- The ADC's digital output, $d = D_{n-1}D_{n-2} \dots D_0$, is given as

$$d = \text{floor}\left[\frac{V_{in}}{\text{step size}}\right]$$

- The **step size (resolution)** is the smallest change in input that can be discerned by the ADC:


$$\text{step size} = \frac{V_{ref}}{2^n}$$

ADC input-output characteristics

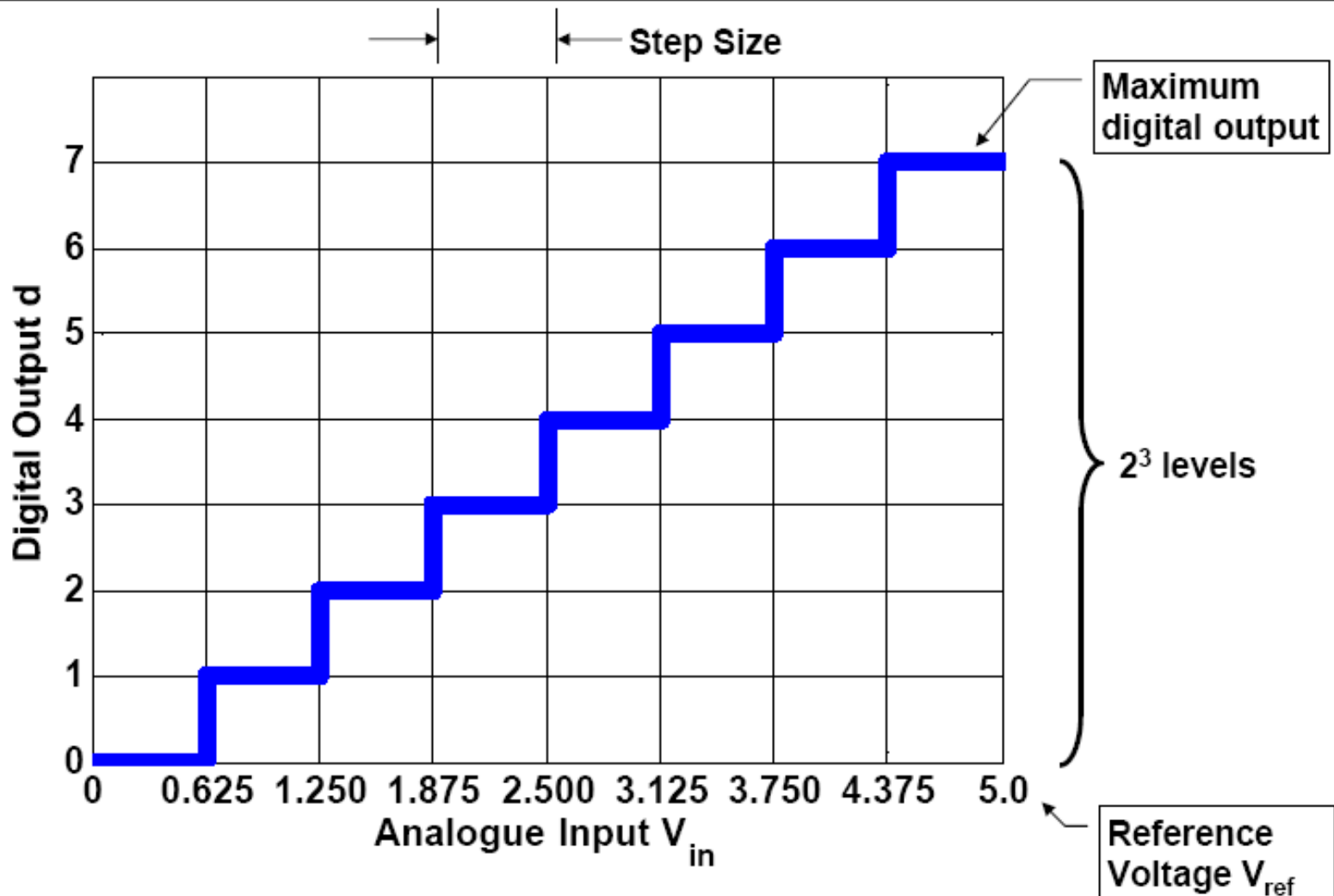


3-bit analogue to digital converter

Sampling an analogue signal

 

Quantizing a sampled signal


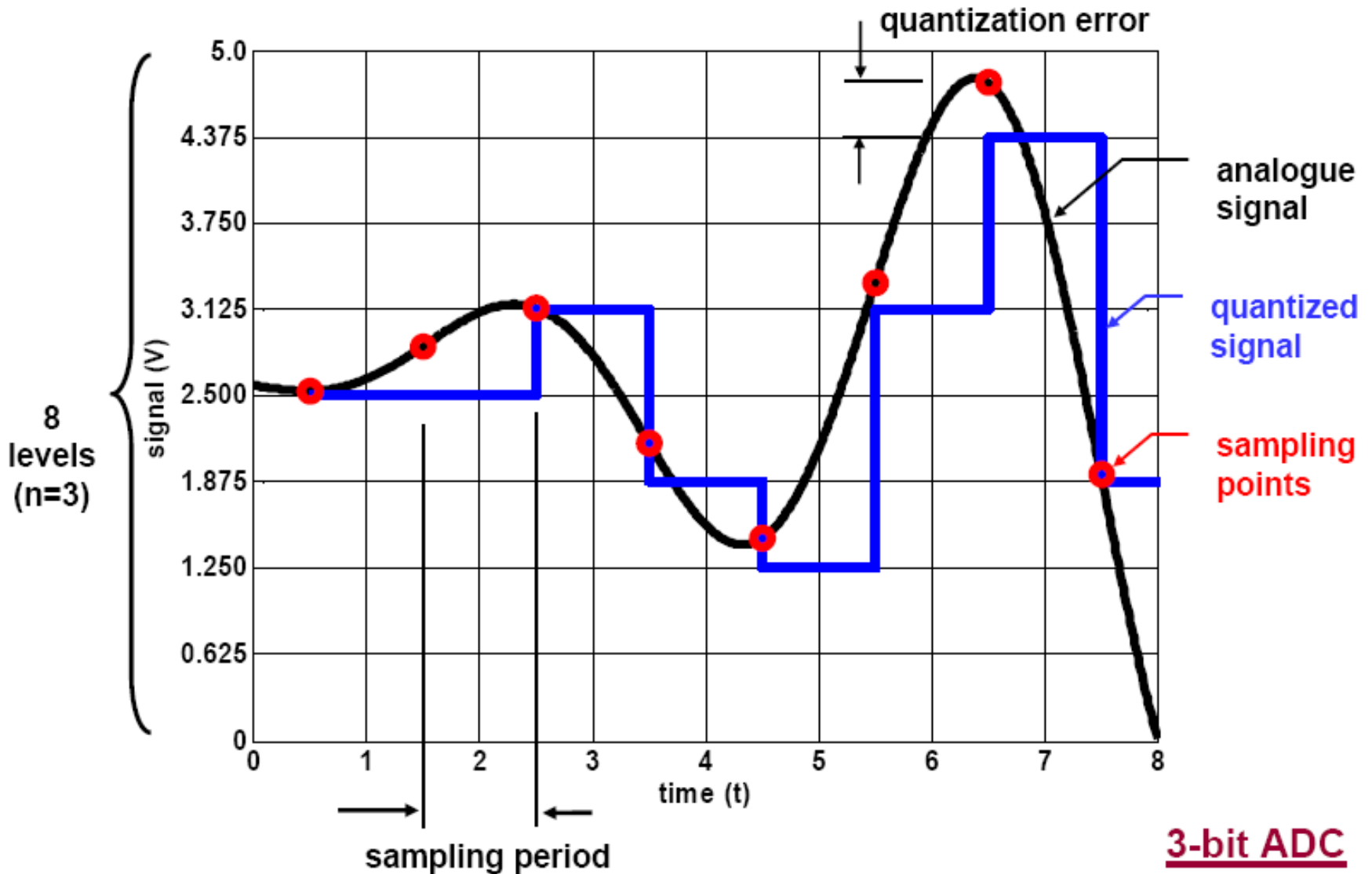


Parameters of an ADC

- **Number of bits n** : The higher the number of bits, the more precise the digital output.
- **Quantisation error E_q** : the average difference between the analogue input and the quantized value. The quantization error of an ideal ADC is half of the step size.
- **Sample time T_{ASM}** : a sampling capacitor must be charged for a duration of t_{ASM} before conversion taking place.
- **Conversion time T_{CONV}** : time taken to convert the voltage on the sampling capacitor to a digital output.


ADC designs: flash ADC

3-bit flash ADC

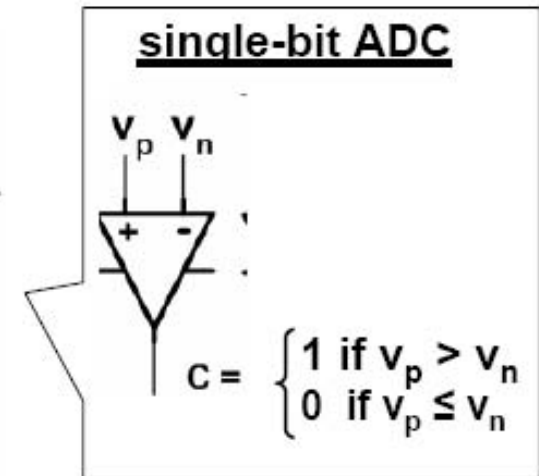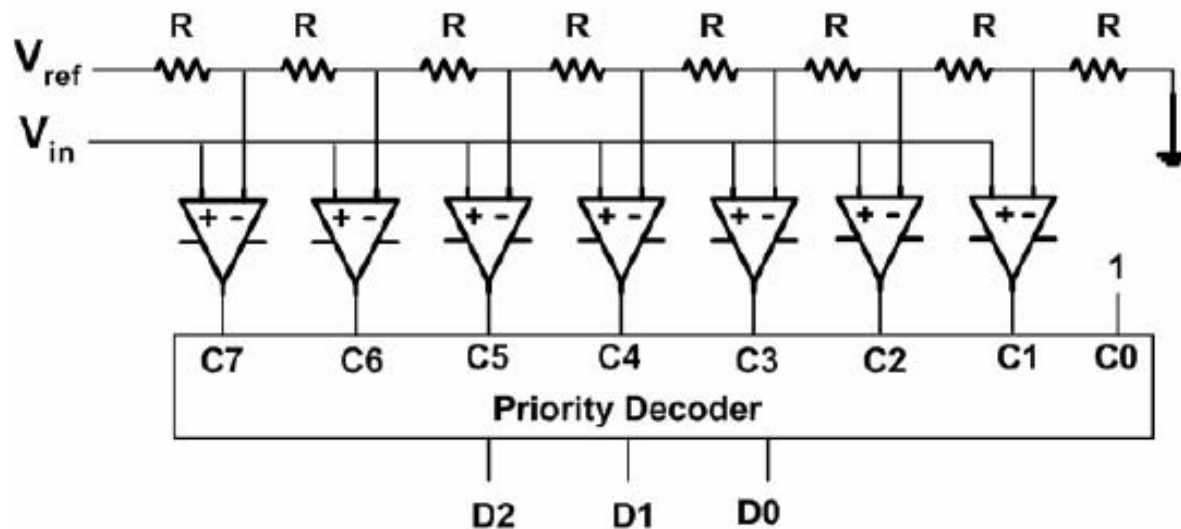

- A n-bit flash ADC uses $2^n - 1$ comparators and a priority decoder.
- **Advantage:** the fastest type of ADC.
- **Disadvantages:** limited resolution, expensive, and large power consumption.

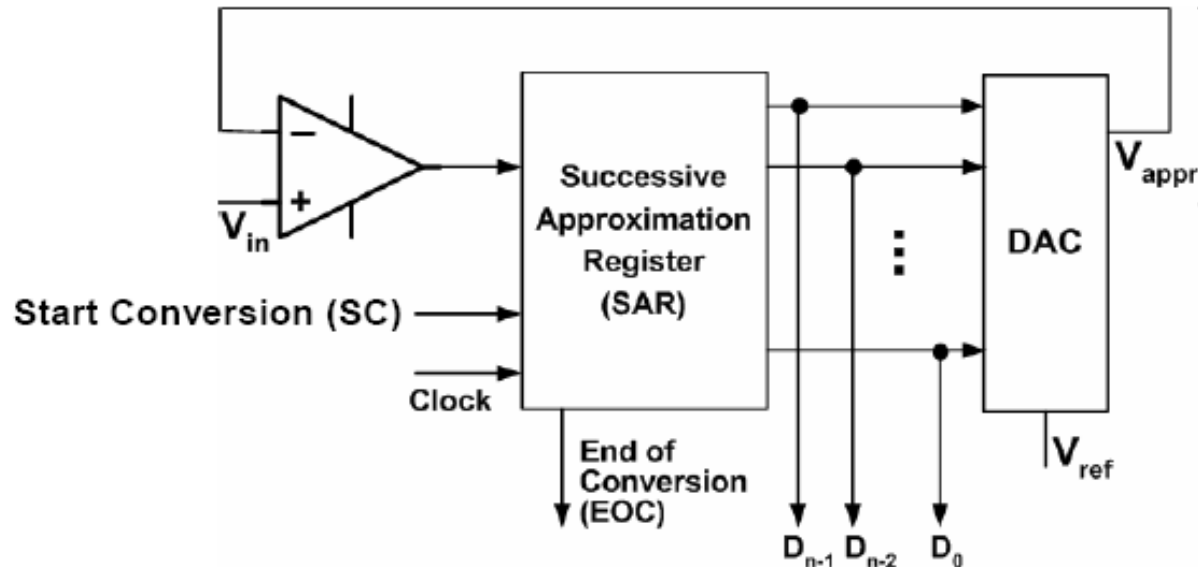
ADC designs: successive-approximation ADC



- Quite fast, one of the most widely used design for ADCs.
- A DAC is used to generate approximations of the input voltage.
- A comparator is used to compare V_{in} and V_{appr} .
- In each cycle, SAR finds one output bit using comparator's output.
- To start conversion, set $SC = 1$. When conversion ends, $EOC = 1$.

Successive-approximation ADC

Binary search for a 3-bit ADC

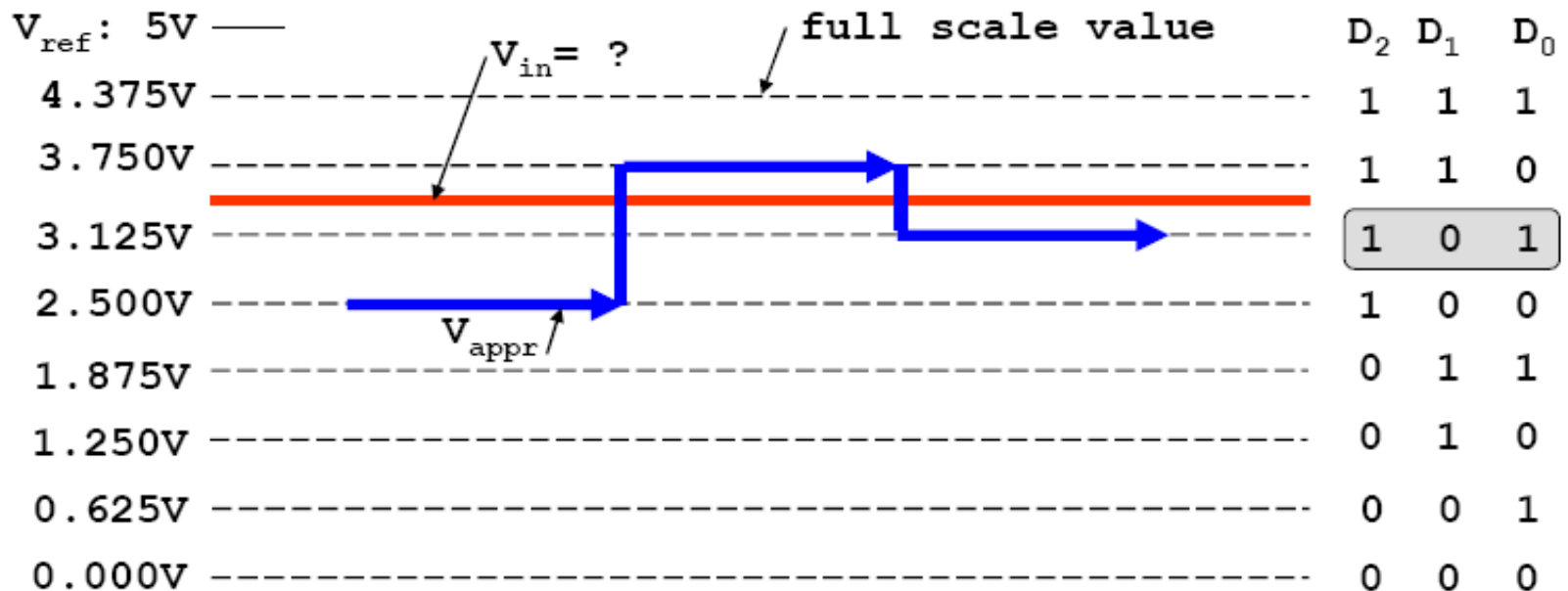


clock cycle 1	clock cycle 2	clock cycle 3
$D_2 = 1$	$D_1 = 0$	$D_0 = 1$
$[V_{in} > V_{appr}]$	$[V_{in} < V_{appr}]$	$[V_{in} > V_{appr}]$


Example of ADC ICs

ADC0804

(National Semiconductor)

 

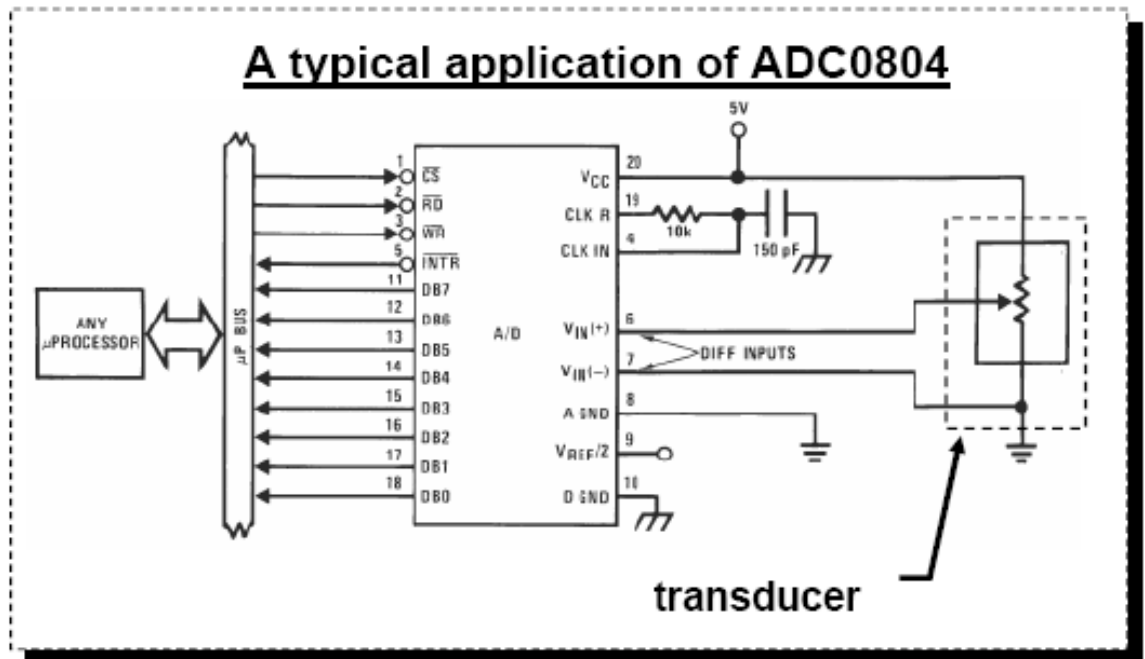- V_{CC}: reference voltage
- RD: to read digital output
- WR: to start a new conversion
- INTR: when conversion completes
- V_{IN}(+), V_{IN}(-): analogue input
- DB0-DB7: 8-bit output
- CLK IN, CLK R: clock signal



Analog to Digital

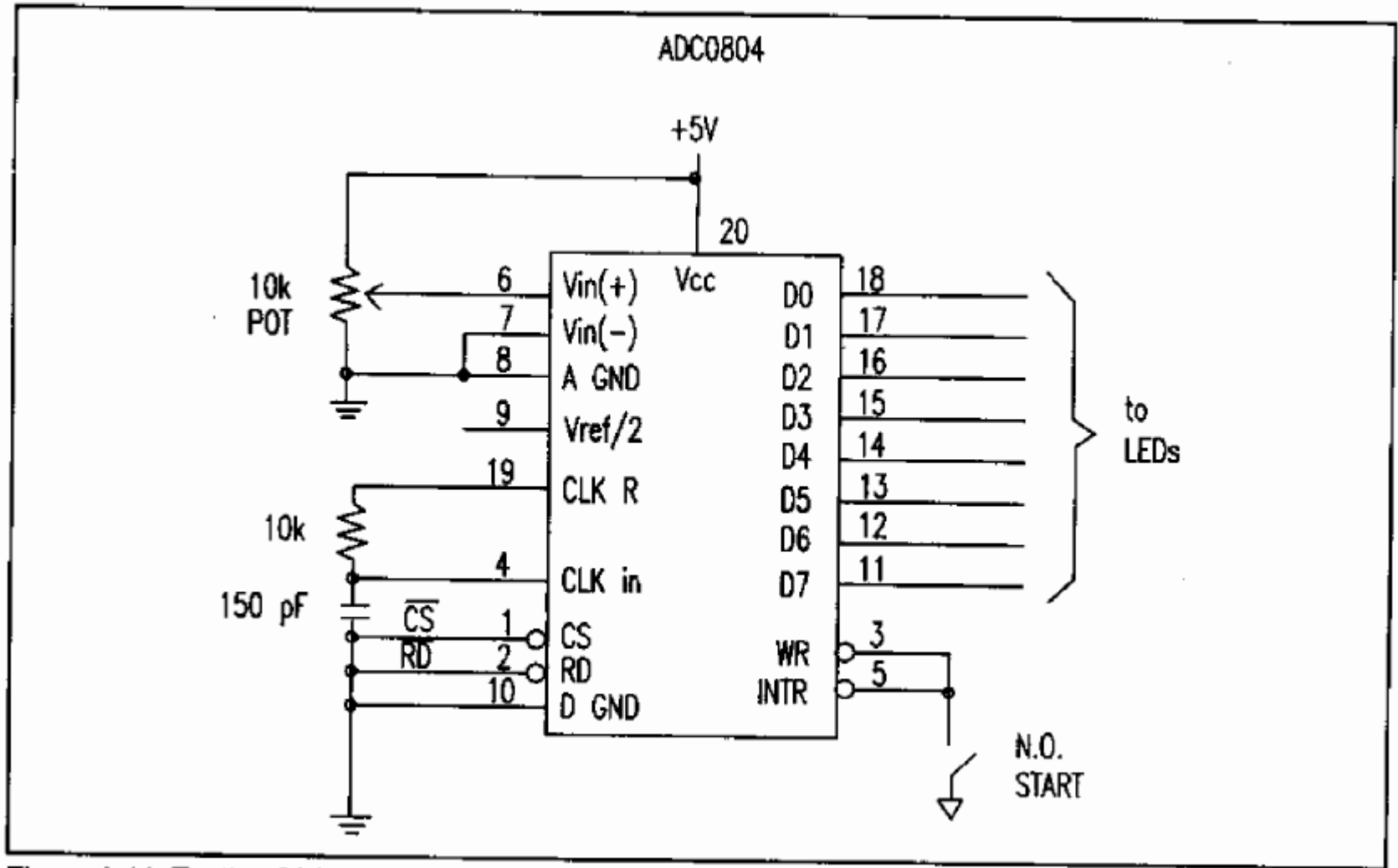


Figure 4-44. Testing 804 in Free Running Mode

V_{in} Range


Table 4-16: $V_{ref}/2$ Relation to V_{in} Range

$V_{ref}/2(V)$	$V_{in}(V)$	Step Size (mV)
not connected*	0 to 5	$5/256 = 19.53$
2	0 to 4	$4/255 = 15.62$
1.5	0 to 3	$3/256 = 11.71$
1.28	0 to 2.56	$2.56/256 = 10$
1	0 to 2	$2/256 = 7.81$
0.5	0 to 1	$1/256 = 3.90$

Notes: $V_{CC} = 5V$

* When not connected (open), $V_{ref}/2$ is measured at 2.5 volts for $V_{CC}=5V$.
Step size (resolution) is the smallest change that can be discerned by an ADC.

Timing Diagram for ADC transaction

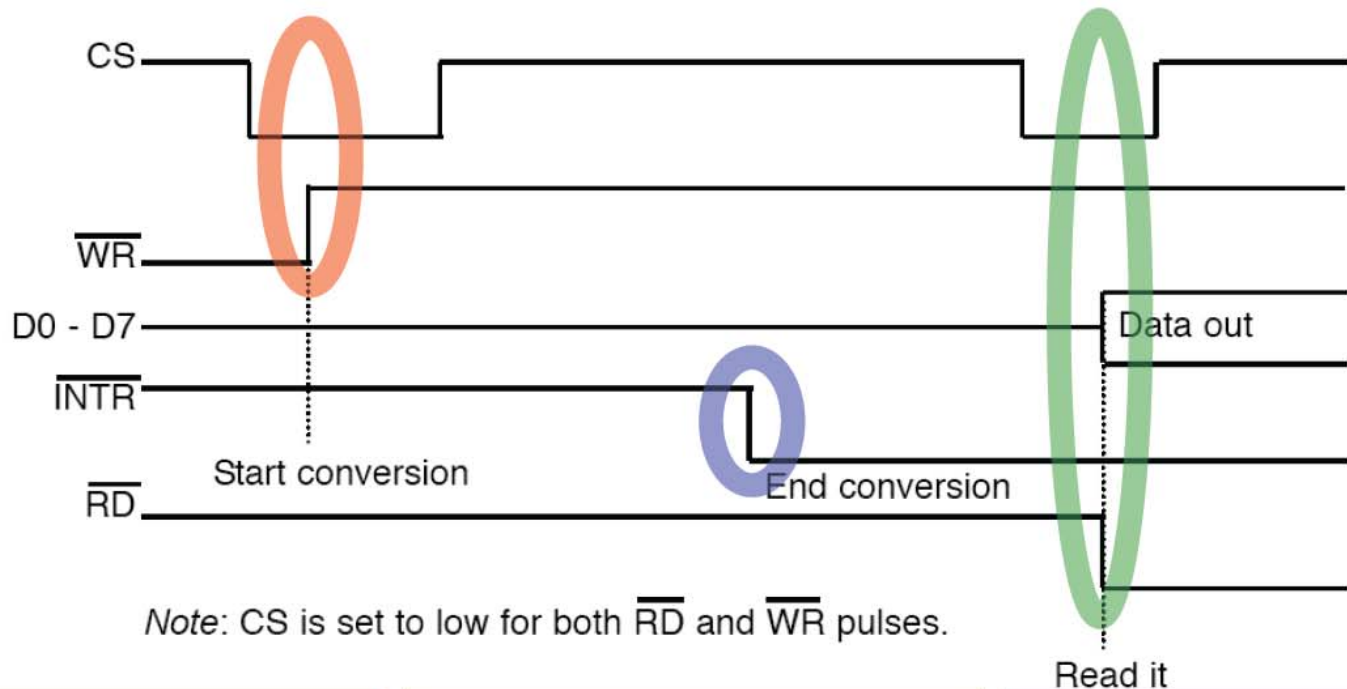

1. rising \overline{WR}
during \overline{CS}

2. ADC finishes
conversion

3. assert \overline{RD}
during \overline{CS}

Could also assert \overline{CS} the whole time w/out pulsing!

CLK IN and CLK R

- As internal clock
- Set the R, C value

$$f = 1/(1.1 RC)$$


- $R = 10K\Omega, C = 150pF$

$$f = 1/(1.1 * 10^4 * 150 * 10^{-12})$$

$$= 606060.6 \Rightarrow 606KHz,$$


or $1.65\mu s$ cycle time

- Can also take external clock

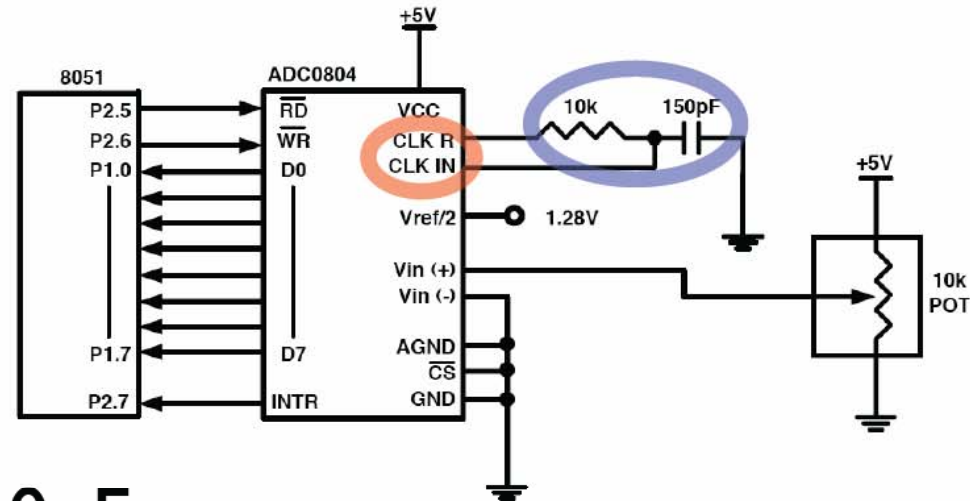

External clocking scheme for ADC0804

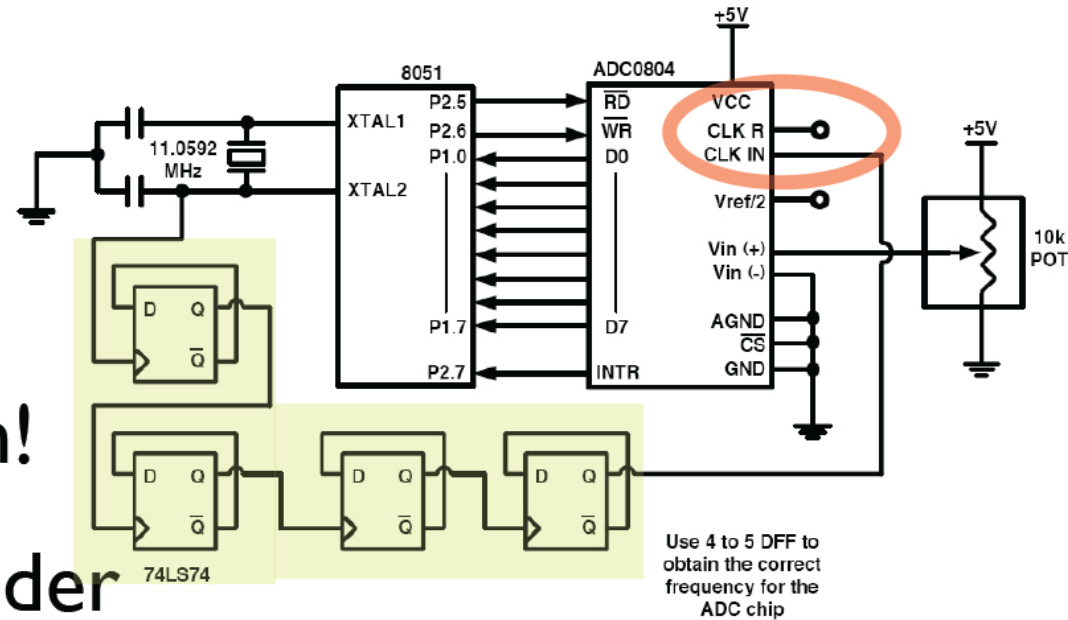
- Could use the same crystal as for 8051
- Issue: freq too high!
- Solution: clock divider



- cascaded D-flipflops:
next one is clocked by the prev's Q,
each feeds /Q to its own D

Assembly for ADC0804

RD	BIT P2.5
WR	BIT P2.6
INTR	BIT P2.7
MYDATA	EQU PI

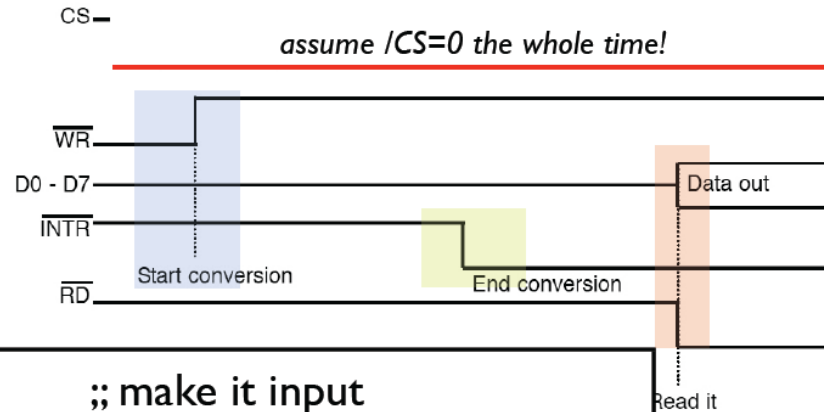

```

        SETB    INTR                ;; make it input
BACK:   CLR     WR                  ;; pulse WR by lowering first
        SETB    WR                  ;; conv starts on rising edge
HERE:   JB     INTR, HERE           ;; poll for /INR to go low
        CLR     RD                  ;; assert output enable
        MOV     A, MYDATA           ;; read conv value from port
        ACALL   CONVERSION          ;; Chap.6 routine to ASCII
        ACALL   DATA_DISPLAY      ;; Chap. 12 routine to display
        SETB    RD                  ;; de-assert output enable
        SJMP   BACK                ;; do it again
    
```

Interfacing ADC

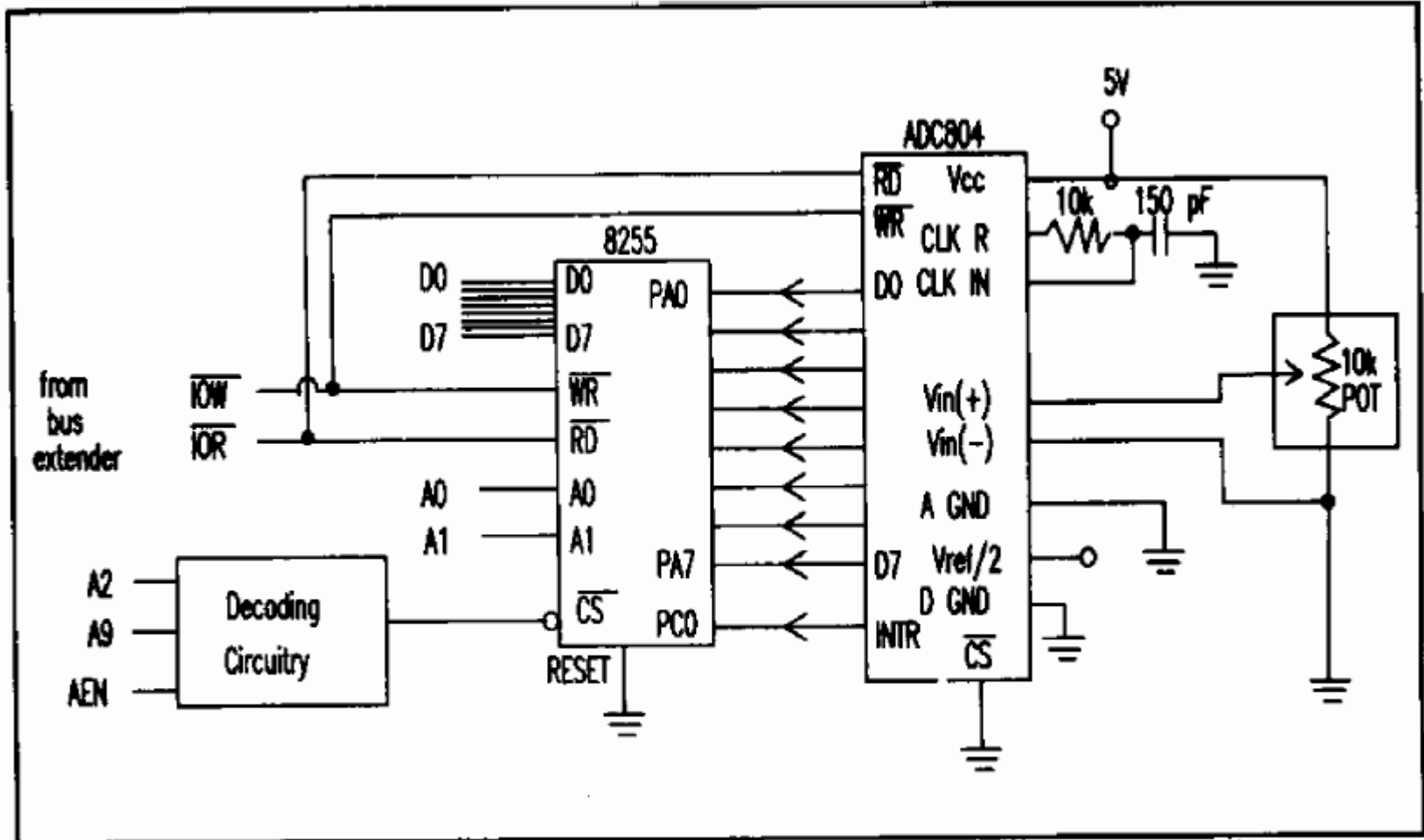


Figure 4-46. 8255 Connection to ADC804

Example (với 80x86)


Example 4-20

Examine the ADC804 connection to the 8255 of the PC Interface Trainer in Figure 4-46. Write a program to monitor INTR and bring in analog input into register AL.

Solution:

```
MOV AL,99H      ;ports A and C as input
MOV DX,303H     ;control port address of PC Trainer
OUT DX,AL       ;initialize ports
AI: MOV DX,302H  ;port C address of PC Trainer
IN AL,DX        ;get INTR status
AND AL,00000001 ;mask all except PC0
CMP AL,00000001 ;is it end of conversion (or INTR low)?
JE AI           ;if no keep checking PC0
;the conversion is finished, next get the data from port A
MOV DX,300H     ;port A address of PC Trainer
IN AL,DX        ;8-bit binary data representing analog input
                ;now AL has the analog input
```

8051 giao tiếp với ADC

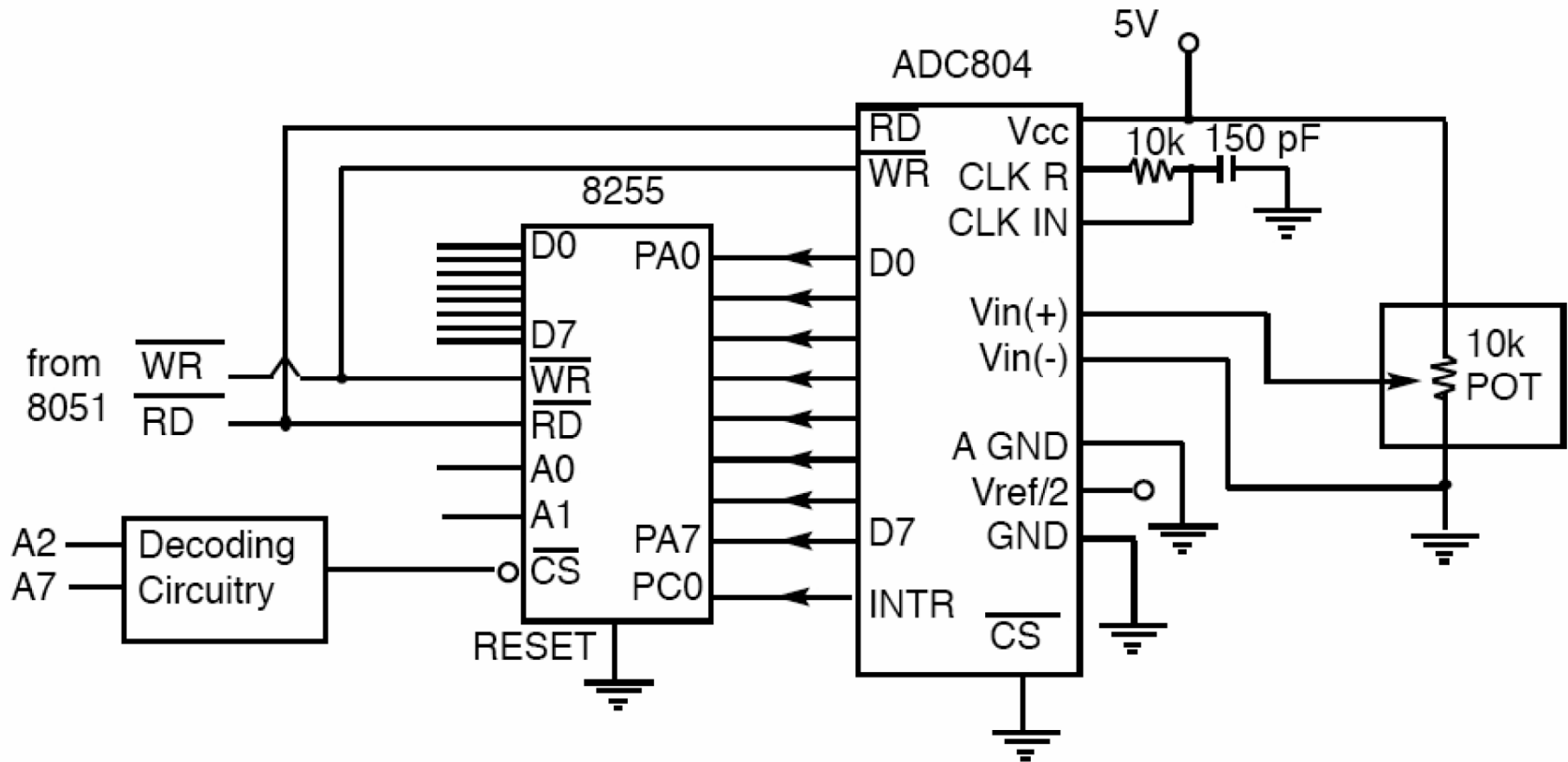

Temperature Sensor

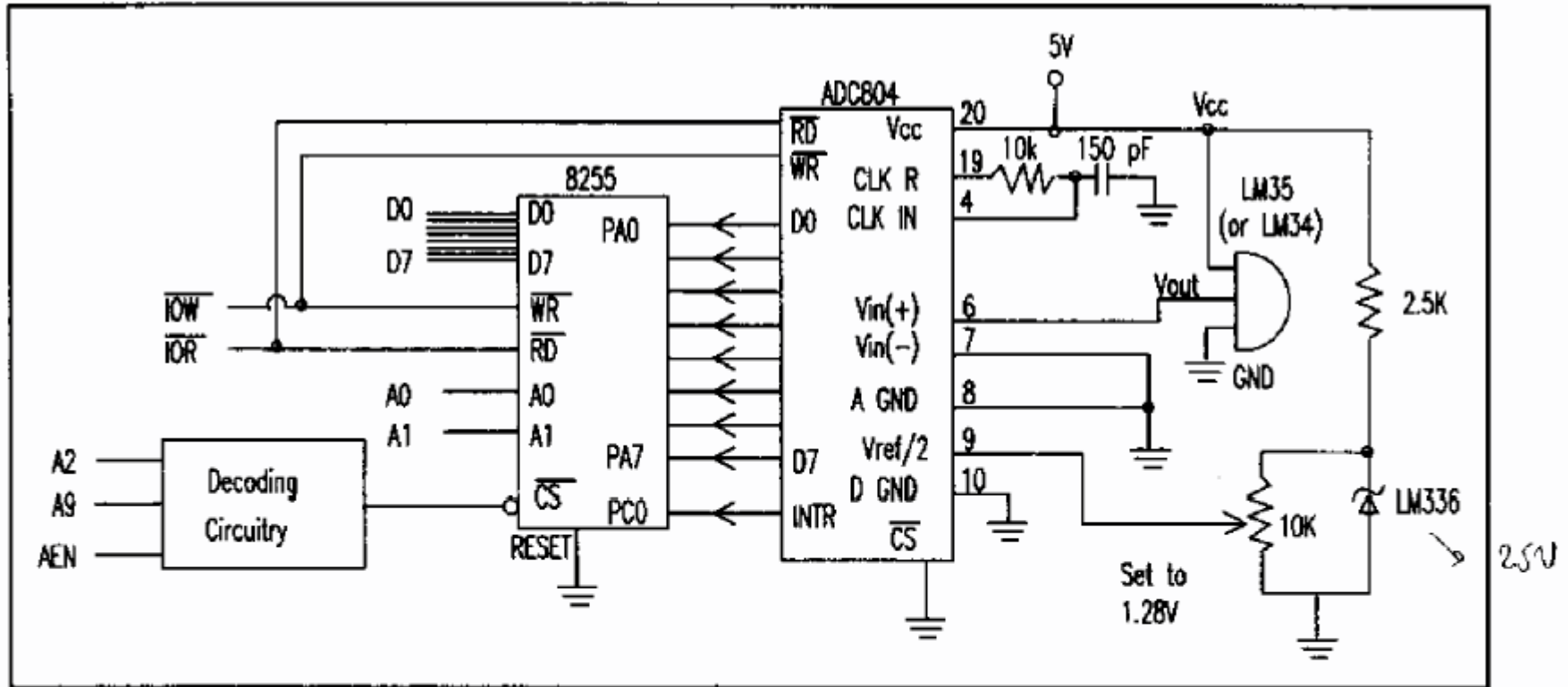


Figure 4-47. Temperature Sensor Connection to ADC804

Table 4-20: Temp. vs. V_{OUT} of the 804


Temperature (C)	V _{in} (mV)	ADC804 V _{out}	
		D7	D0
0	0	0000	0000
1	10	0000	0001
2	20	0000	0010
3	30	0000	0011
10	100	0000	1010
30	300	0001	1110

ADC0808/0809: multi-(analog)-channel


- 8 analog input lines
 - Selected by 3-bit, internally share 1 ADC
 - Conceptually, analog multiplexor on input
 - ALE latches the address
- 8-bit output port
 - similar to the single-channel ADC

Pin interface on ADC0808/0809

 - IN0..IN7: analog input channels
- SC, EOC: (=WR, INTR)
start conv, end-of-conv
- OE: (=RD) output enable
- C B A : 3-bit channel select
- ALE: clock for latching CBA
- $V_{ref}(+), V_{ref}(-)$: max and "gnd"



Timing Diagram for the ADC0809

 


1. set ADDR,
pulse ALE

2. pulse SC,
wait for EOC

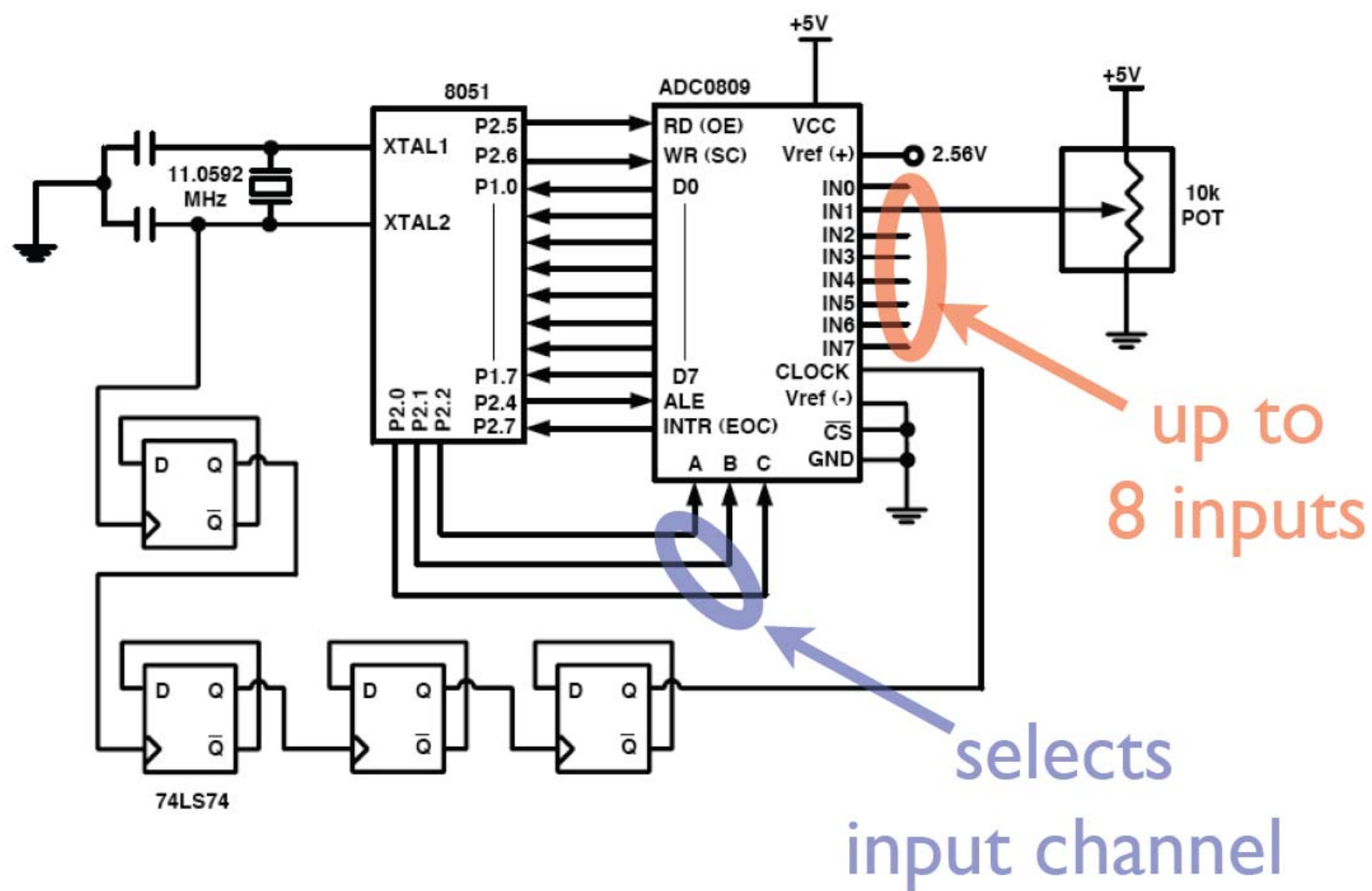3. read data
during OE

ADDR is formed by C B A

Schematic for 8051 connected to ADC0809 up to 8 inputs selects input



Reference voltages


- $V_{\text{ref}}/2$ (e.g., *ADC0804*): half the max voltage
e.g., $V_{\text{ref}}/2=2.5\text{V} \Rightarrow \text{max voltage} = 5.0\text{V}$
 \Rightarrow each step is $5.0\text{V} / 2^8 = 19.53\text{mV}$
- Assumes same GND as signal source
- $V_{\text{ref}}(+), V_{\text{ref}}(-)$ (e.g., *ADC0808/0809*)
 - $V_{\text{ref}}(-)$ serves as GND for signal source
possible to tie $V_{\text{ref}}(-)$ to same GND
 - voltage step = $(V_{\text{ref}}(+)-V_{\text{ref}}(-)) / 2^8$

Single-ended vs Differential Pair input

- Single ended: relative to (common) GND
 - Problem: ground noise, $\sim 10\text{mV}$
- Differential pair: $V_{\text{in}(+)}, V_{\text{in}(-)}$
 - Advantages: no ground noise,
also "common mode noise rejection"

Digital vs Analog Ground

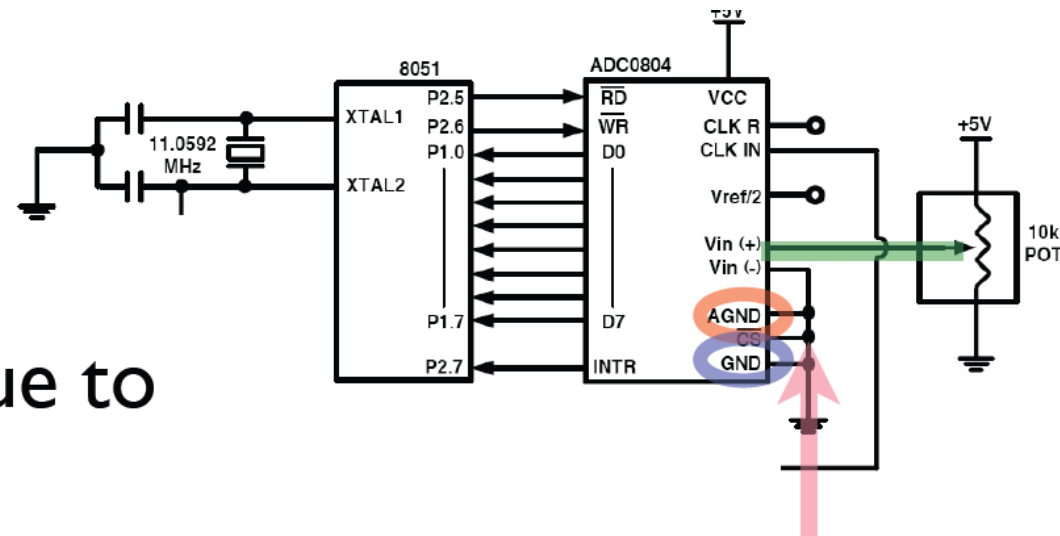
- **AGND**: analog
- **GND**: digital
- Digital => noisy due to frequent switching
- Analog: sensitive to noise
- Solution: separate AGND & GND
- Keep **analog signal** lines short



bad idea
to tie them
together!

Assembly for ADC0809

ALE	BIT P2.4
OE	BIT P2.5
SC	BIT P2.6
EOC	BIT P2.7
ADDR_A	BIT P2.0
ADDR_B	BIT P2.1
ADDR_C	BIT P2.2
MYDATA	EQU P1
ORG	0H
SETB	EOC ;; inp
CLR	ALE
CLR	SC
CLR	OE

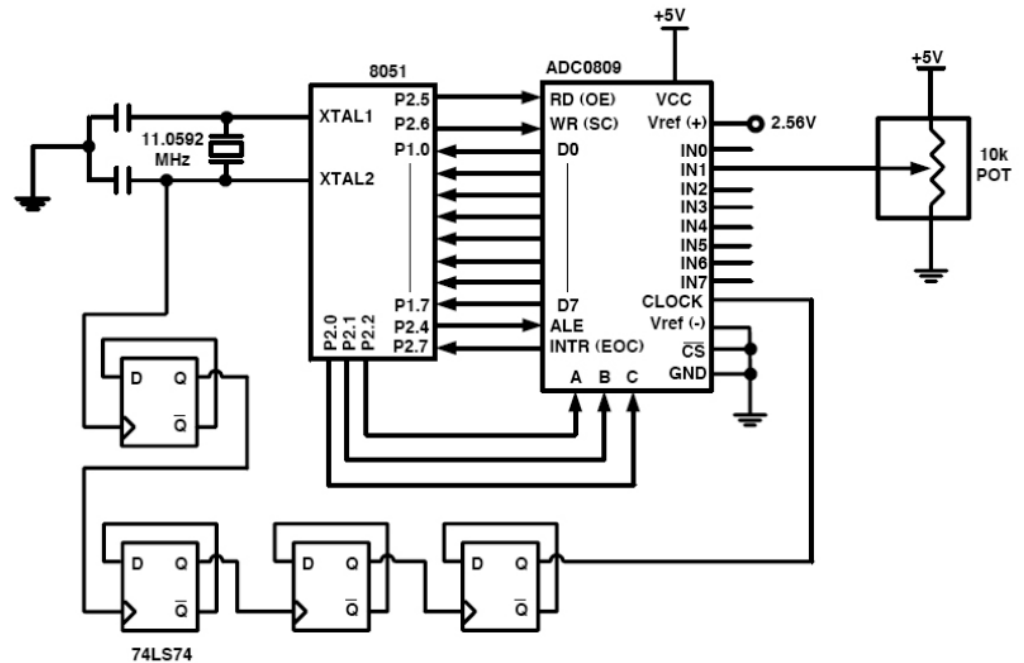

Assembly for ADC0809 (2/2)

BACK:	CLR	ADDR_C	
	CLR	ADDR_B	:: sel ch=1
	SETB	ADDR_A	
	ACALL	DELAY	
	SETB	ALE	:: latch addr
	ACALL	DELAY	
	SETB	SC	:: start
	ACALL	DELAY	
	CLR	ALE	
	CLR	SC	

HERE:	JB	EOC, HERE	
HEREI:	JNB	EOC, HEREI	
	SETB	OE	
	ACALL	DELAY	
	MOV	A, MYDATA	
	CLR	OE	
	ACALL	CONVERSION	
	ACALL	DATA_DISPLAY	
	SJMP	BACK	

Table 10-6: DB-25**Printer Pins**

Pin	Description
1	Strobe
2	Data bit 0
3	Data bit 1
4	Data bit 2
5	Data bit 3
6	Data bit 4
7	Data bit 5
8	Data bit 6
9	Data bit 7
10	Acknowledge
11	Busy
12	Out of paper
13	Select
14	Auto feed
15	Error
16	Initialize printer
17	Select input
18	Ground
19	Ground
20	Ground
21	Ground
22	Ground
23	Ground
24	Ground
25	Ground

Printer Connection

 


Figure 10-8. DB-25P (Male) Printer Connector
 (Reprinted by permission from "IBM Technical Reference" c. 1988
 by International Business Machines Corporation)

IO Base Address for LPT

- -d 0040:0008
- LPT: 03BC, 0378, 0278
- 3 I/O ports
 - LPT data lines
 - LPT status lines
 - LPT control lines

Table 10-7: BIOS I/O Base Addresses for LPT

I/O Base Address	LPT
0040:0008 - 0040:0009	LPT1
0040:000A - 0040:000B	LPT2
0040:000C - 0040:000D	LPT3
0040:000E - 0040:000F	LPT4

Table 10-8: IBM PC Printer Ports and Their Functions

Line Printer	Data Port (R/W)	Status Port (Read Only)	Control Port (R/W)
LPT 1	03BCH	03BDH	03BEH
LPT 2	0378H	0379H	037AH
LPT 3	0278H	0279H	027AH

Printer's Ports

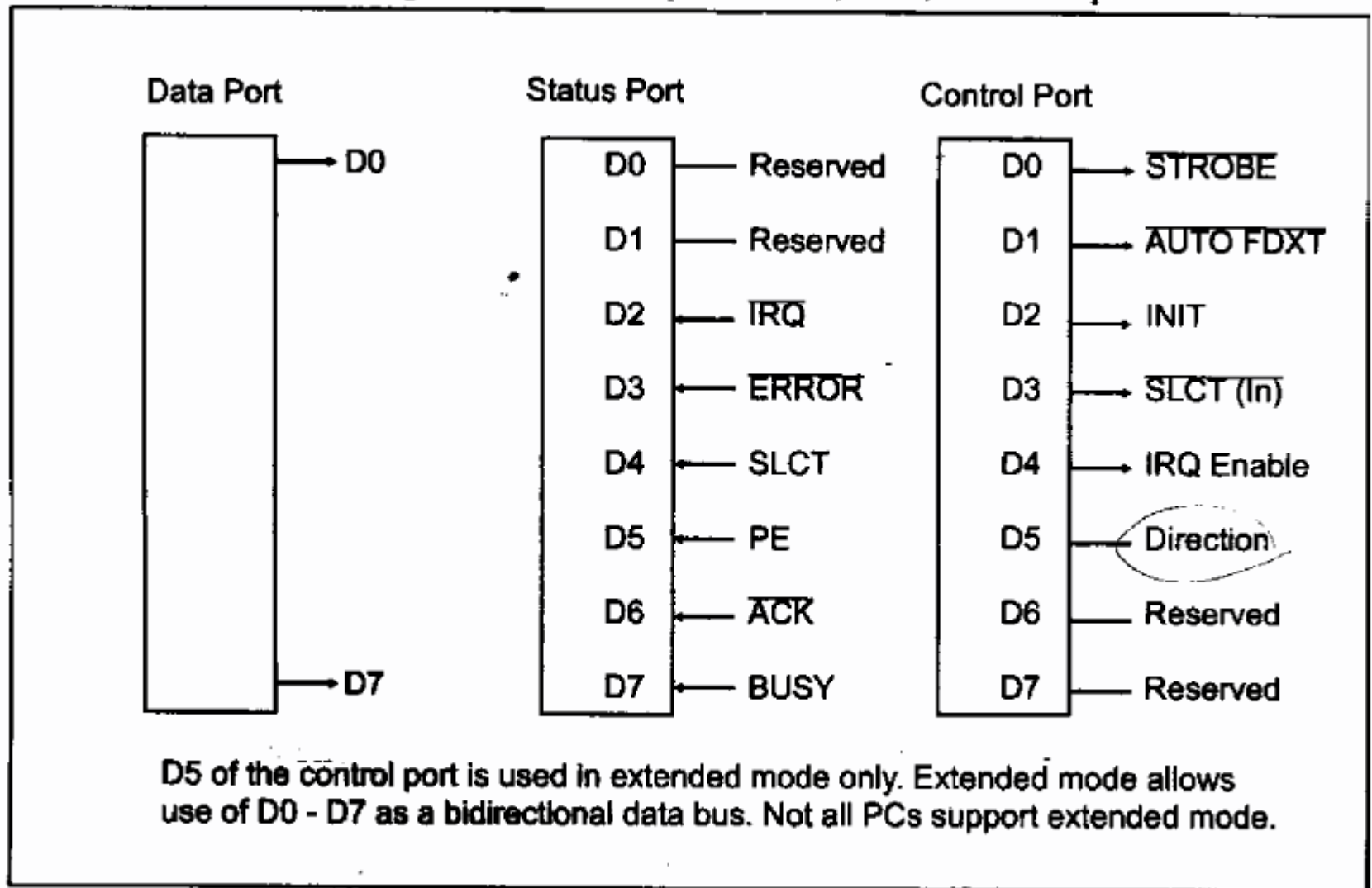


Figure 10-9. Printer's Data, Status, and Control Ports

Useful Links

- <http://www.kmitl.ac.th/~kswichit/>
- <http://www.8052.com/codelib.phtml>
- <http://www.circuits-city.com/>
- [http://www.ikalogic.com/cat microcontrolle
rs.php](http://www.ikalogic.com/cat_microcontrolle
rs.php)